# 0.1 VTU Question Papers

2020-JULY-6b, For the circuit shown in Figure 1 find i)  $i(0+),\;v(0+),\frac{di(0+)}{dt},\frac{dv(0+)}{dt},\;i(\infty),\;v(\infty)$  .



Figure 1: Example

# Solution:

When the switch is closed at t = 0+ the capacitor acts as short circuit and inductor acts as open circuit which is as shown in Figure 3.



Figure 2: Example

$$i(0+) = 0$$
  
 $v(0+) = 0$ 

$$\frac{di(0+)}{dt} = 0$$
$$\frac{dv(0+)}{dt} = 0$$

When the switch is closed at  $t = \infty$  the capacitor acts as open circuit and inductor acts as short circuit which is as shown in Figure ??.



Figure 3: Example

$$i(\infty) = \frac{12}{6} = 2A$$
$$v(\infty) = 12V$$

2020-Aug JAN-2014) For the circuit shown in Figure 4 switch K is changed from position a to b at t=0, steady state condition having been reached before switching. Find the values of i,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  b at  $t = 0^+$ .



Figure 4: Example

# Solution:

When switch is at position a and reached steady state, which is as shown in Figure 5(a).

$$Ri(0^{-}) = V$$
  
$$i(0^{-}) = \frac{V}{R} = \frac{20}{10} = 2 A$$

When the switch is at position b, the circuit is as shown in Figure 5 (b)



Figure 5: Example

$$Ri + L\frac{di}{dt} + \frac{1}{C}\int idt = 0 \tag{1}$$

At  $t = 0^+$ 

$$Ri(0^{+}) + L\frac{di}{dt}(0^{+}) + \frac{1}{C}\int i(0^{+})dt = 0$$

It is given that capacitor is initially uncharged

$$\frac{1}{C} \int i(0^{+})dt = v_{c}(0^{+})) = 0$$
  

$$Ri(0^{+}) + L\frac{di}{dt}(0^{+}) = 0$$
  

$$10 \times 2 + 1\frac{di}{dt}(0^{+}) = 0$$
  

$$\frac{di}{dt}(0^{+}) = -20 A/sec$$

Differentiating equation 1

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

Substituting initial conditions

$$R\frac{di}{dt}(0^{+}) + L\frac{d^{2}i}{dt^{2}}(0^{+}) + \frac{i(0^{+})}{C} = 0$$
  
$$10 \times (-20) + 1\frac{d^{2}i}{dt^{2}}(0^{+}) + \frac{2}{1 \times 10^{-6}} = 0$$

$$\frac{d^2i}{dt^2}(0^+) = 200 - 2 \times 10^6$$
$$= -1.9998 \times 10^6 A/sec^2$$

JULY-2019-CBCS In the circuit shown in Figure 6 switch S is changed from position a to b at t = 0. Solve for i,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$  if  $R = 100\Omega$ , L = 0.1H and  $C = 0.25\mu F$  and V=100 V. Assume that the capacitor is initially uncharged.



Figure 6: JULY-2019

# Solution:

When the switch is at position a at  $t = 0^{-}$ , inductor acts as a short circuit which is as shown in Figure 7.



Figure 7: JULY-2019

$$\begin{aligned} Ri(0^{-}) &= V \\ i(0^{-}) &= \frac{V}{R} = \frac{100}{100} = 1 \ A \end{aligned}$$

Current through inductor cannot change instantaneously.

$$i(0^+) = i(0^-) = 1 A$$

It is given that capacitor is initially uncharged.

$$v_c(0^-) = 0 = v_c(0^+)V$$

When the switch is at position b, and at  $t = 0^+$ , the circuit is as shown in Figure 8.



Figure 8: JULY-2019 By KVL around the loop

$$Ri + L\frac{di}{dt} + \frac{1}{C}\int idt = 0$$
 (2)

At  $t = 0^+$ 

$$Ri(0^{+}) + L\frac{di}{dt}(^{0}+) + \frac{1}{C}\int i(0^{+})dt = 0$$

It is given that capacitor is initially uncharged

$$\frac{1}{C}\int i(0^+)dt = v_c(0^+) = 0$$

$$Ri(0^{+}) + L\frac{di}{dt}(0^{+}) = 0$$

$$100 \times (1) + L\frac{di}{dt}(0^{+}) = 0$$

$$L\frac{di}{dt}(0^{+}) = -100$$

$$\frac{di}{dt}(0^{+}) = \frac{-100}{0.1}$$

$$= -1000 \ A/sec$$

Differentiating equation 2

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

Substituting initial conditions

$$L\frac{d^{2}i}{dt^{2}}(0^{+}) = -R\frac{di}{dt}(0^{+}) - \frac{i(0^{+})}{C}$$
  

$$0.1\frac{d^{2}i}{dt^{2}}(0^{+}) + = -100 \times (-1000) - \frac{1}{0.25 \times 10^{-6}}$$
  

$$0.1\frac{d^{2}i}{dt^{2}}(0^{+}) = 0.1 \times 10^{6} + 4 \times 10^{6}$$
  

$$\frac{d^{2}i}{dt^{2}}(0^{+}) = 39 \times 10^{6} A/sec^{2}$$

JULY-2018-CBCS The switch in the network shown in Figure 9 is closed at t = 0. Determine the voltage across the capacitor.



Figure 9: 2018-CBCS-Question Paper

# Solution:

Before closing the switch at  $t = 0^-$  the voltage across the capacitor is

$$v_c(0^-) = i(0^-)R_2 \tag{3}$$

The switch is closed at t = 0 at  $t = 0^+$ 

$$v_c(0^+) = i(0^+)10$$
  
 $v_c(0^+) = \frac{10}{10+10} \times 10$   
 $= 5V$ 

JAN-2017-CBCS In the circuit shown in Figure 10 V=10 v  $R = 10 \ \Omega \ L = 1 \ H$  and  $C = 10 \ \mu F$  and  $v_c(0) = 0$ , find  $i(0^+)$ ,  $\frac{di}{dt}(0^+)$  and  $\frac{d^2i}{dt^2}(0^+)$ .



Figure 10: 2017-CBCS-Question Paper Solution:

The switch is closed at  $t = 0^+$  the inductor acts as open circuit and capacitor acts as short circuit which is as shown in Figure 11. At  $t = 0^-$ ,  $i(0^-) = i(0^+) = 0$ 



Figure 11: Example

$$Ri + L\frac{di}{dt} + \frac{1}{C}\int idt = 10 \tag{4}$$

At  $t = 0^+$ 

$$Ri(0^+) + L\frac{di}{dt}(0^+) + \frac{1}{C}\int i(0^+)dt = V$$
$$\frac{di}{dt}(0^+) = \frac{V}{L}$$
$$= 10A/sec$$

Differentiating equation 4

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0 \tag{5}$$

Substituting initial conditions

$$R\frac{di}{dt}(0^+) + L\frac{d^2i}{dt^2}(0^+) + \frac{i(0^+)}{C} = 0$$
 (6)

$$L\frac{d^{2}i}{dt^{2}}(0^{+}) = -10 \times 10 - \frac{i(^{0}+)}{C}$$
  

$$1\frac{d^{2}i}{dt^{2}}(0^{+}) = 100 - \frac{0}{C}$$
  

$$\frac{d^{2}i}{dt^{2}}(0^{+}) = -100A/sec^{2}$$

2020-July-5b-CBCS JAN-2017-6b-CBCS In the network shown in Figure 12 a steady state is reached with the switch K open. At t=0, the switch is closed. For the given element values, determine  $v_a(0^-)$  and  $v_a(0^+)$ 



Figure 12: 2017-CBCS-Question Paper

Solution:

When switch is opened and steady state reached inductor acts as short circuit which is as shown in Figure 13 (a)



Figure 13: 2017-CBCS-Question Paper

$$\frac{V_a(0^-) - 5}{10} + \frac{V_a(0^-) - V_b(0^-)}{20} = 0$$

$$V_a(0^-) \left[\frac{1}{10} + \frac{1}{20}\right] = \frac{5}{10}$$

$$V_a(0^-) = \frac{0.5}{0.15} = 3.333V$$
(07) and (

$$i_L(0^-) = i_L(0^+) = [0.15] = \frac{V_a(0^-)}{20} + \frac{5}{10} = 0.667A$$

When switch is closed, 10  $\Omega$  resistor is connected to a point  $v_a$  steady state reached inductor acts as short circuit which is as shown in Figure 13 (b)

$$\frac{v_a - 5}{10} + \frac{v_a - v_b}{20} + \frac{v_a}{10} = 0$$
  
$$v_a(0^+) \left[ \frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right] - \frac{v_b}{20} = \frac{5}{10}$$
  
$$0.25v_a(0^+) - 0.05v_b(0^+) = 0.5$$

$$\frac{v_b - v_a}{20} + \frac{v_b - 5}{10} + i_L = 0$$
  
-0.05v\_a(0<sup>+</sup>) + 0.15v\_b(0+) = 0.5 - 0.667A  
-0.05v\_a(0<sup>+</sup>) + 0.15v\_b(0+) = -0.1667

JAN-2017-NON-CBCS For the circuit shown in Figure 14 the switch S is changed from position 1 to 2 at t = 0. The circuit was under steady state before this action. Determine the value v and i at  $t = 0^+$  and their first and second derivatives.



Figure 14: Example

#### Solution:

When switch was at position 1 at  $t = 0^-$ , under steady state condition capacitor charges with voltage of  $v(0^-) = 50 = v(0^+)$  and after that it acts as an open circuit which is as shown in Figure 15



Figure 15: Example

At  $t=0^-$  , inductor is in open circuit and capacitor is after fully charging it is also in open circuit state. That is

$$i(0^{-}) = 0$$
 and also  $i(0^{+}) = 0$  (7)

When switch is at position 2, and at  $t = 0^+$  the circuit diagram is as shown in Figure 15

Applying KVL for the circuit we have

$$Ri + L\frac{di}{dt} + \frac{1}{C}\int idt = 0$$
$$Ri + L\frac{di}{dt} + v_c(t)dt = 0$$

At  $t = 0^+$  and  $v_c(0^+) = 50$ 

$$Ri(0^{+}) + L\frac{di}{dt}(0^{+}) + v_{c}(0^{+}) = 0$$
  
$$20 \times 0 + 2\frac{di}{dt}(0^{+}) + 50 = 0$$
  
$$\frac{di}{dt}(0^{+}) = \frac{-50}{2} = -25$$

Differentiating equation (1)

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0 \tag{8}$$

Substituting initial conditions

$$R\frac{di}{dt}(0^{+}) + L\frac{d^{2}i}{dt^{2}}(0^{+}) + \frac{i(0^{+})}{C} = 0$$
  
$$20 \times (-25) + 2\frac{d^{2}i}{dt^{2}}(0^{+}) + \frac{0}{C} = 0$$
  
$$\frac{d^{2}i}{dt^{2}}(0^{+}) = \frac{500}{2} = 250A/sec^{2}$$

July-2016 For the circuit shown in Figure 16 the switch K is changed from position A to B at t=0. After having reached steady state in position A. Find i  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$ ,  $and \frac{d^3i}{dt^3}$  at t=0+.



# Figure 16: Example

## Solution:

Before connecting to position B switch was at position A at t=0- under steady state condition capacitor charges with voltage of v(0-) = 100 =v(0+) and after that it acts as an open circuit which is as shown in Figure 17(a)



Figure 17: Example

At t = 0- , inductor is in short circuit and capacitor is after fully charged and it is also in open circuit state.

$$i(0-) = 0$$
 and also  $i(0+) = 0$  (9)

When switch is at position B, and at t=0+ the circuit diagram is as shown in Figure 15 (b)

Applying KVL for the circuit we have

$$L\frac{di}{dt} + \frac{1}{C}\int idt = 0$$
$$L\frac{di}{dt} + v_c(t)dt = 0$$

At t = 0+ and  $v_c(0+) = 100$ 

$$L\frac{di}{dt}(0+) + v_c(0+) = 0$$
  
$$1\frac{di}{dt}(0+) + 100 = 0$$
  
$$\frac{di}{dt}(0+) = -100$$

Differentiating equation (1)

$$L\frac{d^2i}{dt^2} + \frac{i}{C} = 0 \tag{10}$$

<sup>2</sup> Substituting initial conditions

$$\begin{aligned} \frac{d^2i}{dt^2}(0+) + \frac{i(0+)}{C} &= 0\\ 1\frac{d^2i}{dt^2}(0+) + \frac{0}{C} &= 0\\ \frac{d^2i}{dt^2}(0+) &= 0A/sec^2\\ \frac{d^3i}{dt^3}(0+) &= 0A/sec^2 \end{aligned}$$

July-2016-2 For the circuit shown in Figure 18 the switch K is opened at t=0. Find i  $\frac{di}{dt}$ ,  $v_c$ ,  $\frac{dv_c}{dt}$  at t=0+.



Figure 18: Example

Solution: When switch is at position a at t=0-



# Figure 19: Example

When switch is at opened, at t=0+ circuit which is as shown in Figure 19 (a)

$$V = Ri(0-) \tag{11}$$

$$i(0-) = \frac{V}{R} = \frac{4}{2} = 2 A \tag{12}$$

When switch is at opened, at t=0+ circuit which is as shown in Figure 19 (b)

Applying KVL

$$V = \frac{1}{C} \int i dt + L \frac{di}{dt} + Ri \tag{13}$$

At t=0+

$$2 = 0 + 1 \times \frac{di(0+)}{dt} + 1 \times i(0+) \tag{14}$$

$$2 = 0 + 1 \times \frac{di(0+)}{dt} + 1 \times i(0+)$$
$$\frac{di}{dt}(0+) = 2 - 1 \times 2 = 0$$

The voltage across capacitor is

$$v_c(t) = \frac{1}{C} \int i$$

$$\frac{dv_c(t)}{dt} = \frac{1}{C}i$$

$$\frac{dv_c(t)}{dt}(0+) = \frac{1}{C}i(0+)$$

$$\frac{dv_c(t)}{dt}(0+) = \frac{1}{1}2 = 2V$$
(15)

July-2015-6-b For the circuit shown in Figure 20 the switch K is opened at t = 0 after reaching the steady state condition. Determine voltage across switch and its first and second derivatives at  $t = 0^+$ .



Figure 20: Example

Solution: Before opening switch and at t=0-

circuit diagram is as shown in Figure 21 (a)



Figure 21: Example

$$V = Ri(0-)$$
  
$$i(0-) = \frac{V}{R} = \frac{2}{1} = 2 \ A = i(0+)$$

When switch is opened at t=0+ circuit diagram is as shown in Figure 21 (b)

Applying KVL

$$V = \frac{1}{C} \int i dt + L \frac{di}{dt} + Ri \tag{16}$$

At t=0+

$$2 = 0 + 1 \times \frac{di(0+)}{dt} + 1 \times i(0+) \tag{17}$$

$$\begin{array}{rcl} 2 & = & 0+1\times \frac{di(0+)}{dt} + 1\times i(0+) \\ \\ \frac{di}{dt}(0+) & = & 2-1\times 2 = 0 \end{array}$$

Differentiating Equation 16

Differentiating Equation 16

$$0 = \frac{1}{C}\frac{di}{dt} + L\frac{d^{3}i}{dt^{3}} + R\frac{d^{2}i}{dt^{2}}$$
$$1 \times \frac{d^{3}i_{1}}{dt^{3}}(0+) = -R\frac{d^{2}i(0+)}{dt^{2}} - \frac{1}{C}\frac{d(0+)i}{dt}$$
$$\frac{d^{3}i(0+)}{d3^{2}} = -1 \times (-4) - 0 = 4 A/sec^{2}$$

The voltage across capacitor is

$$V_k + L\frac{di}{dt} + R \times i = 2 \tag{18}$$

$$\frac{dV_k}{dt} + L\frac{d^2i}{dt^2} + R \times \frac{di}{dt} = 0$$
$$\frac{dv_c(t)}{dt}(0+) = \frac{1}{C}(5-5) = 0$$

Differentiating equation (1)

$$\frac{d^2 V_k}{dt^2} + L \frac{d^3 i}{dt^3} + R \times \frac{d^2 i}{dt^2} = 0$$
(19)

$$\begin{array}{ll} \displaystyle \frac{d^2 V_k(0+)}{dt^2} & = & -L \frac{d^3 i(0+)}{dt^3} + R \times \frac{d^2 i(0+)}{dt^2} \\ \displaystyle \frac{d^2 V_k(0+)}{dt^2} & = & -1 \times 4 - 1 \times (-4) = 0 \ V/sec^2 \end{array}$$

DEC-2015 6-a For the circuit shown in Figure 22 the switch K is changed from position A to B at t=0, the steady state having been reached before switching. Calculate i,  $\frac{di}{dt}$ , and  $\frac{d^2i}{dt^2}$  at t=0+.



Figure 22: Example

#### Solution:

Before connecting to position 2 switch was at position 1 at t=0- under steady state condition capacitor charges with voltage of v(0-) = 50 =v(0+) and after that it acts as an open circuit which is as shown in Figure 23 (a)



Figure 23: Example

At t = 0- , inductor is in open circuit and capacitor is after fully charging it is also in open circuit state. That is

$$i(0-) = 0$$
 and also  $i(0+) = 0$  (20)

When switch is at position 2, and at t=0+ the circuit diagram is as shown in Figure 23 (b)

Applying KVL for the circuit we have

$$Ri + L\frac{di}{dt} + \frac{1}{C}\int idt = 0$$
$$Ri + L\frac{di}{dt} + v_c(t)dt = 0$$

At t = 0+ and 
$$v_c(0+) = 50$$
  
 $Ri(0+) + L\frac{di}{dt}(0+) + v_c(0+) = 0$   
 $20 \times 0 + 1\frac{di}{dt}(0+) + 50 = 0$   
 $\frac{di}{dt}(0+) = \frac{-50}{1} = -50 \ A/sec$ 

Differentiating equation (1)

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0$$
(21)

Substituting initial conditions

$$R\frac{di}{dt}(0+) + L\frac{d^{2}i}{dt^{2}}(0+) + \frac{i(0+)}{C} = 0$$
  
$$20 \times (-50) + 1\frac{d^{2}i}{dt^{2}}(0+) + \frac{0}{C} = 0$$
  
$$\frac{d^{2}i}{dt^{2}}(0+) = \frac{1000}{1} = 1000A/sec^{2}$$

Q DEC-2015 6b) In the circuit shown in Figure 24 the steady state is reached with switch K is open. The switch K is closed at t = 0. Solve for  $i_1, i_2, \frac{di_1}{dt}, \frac{di_2}{dt}$  at t = 0+.



Figure 24: Example

Solution:

When switch is opened and when steady state is reached capacitor acts as open circuit and inductor acts as short circuit which is as shown in Figure 25(a).



Figure 25: Example

$$i_1(0-) = \frac{100}{20+10} = 3.33A$$
  
 $i_2(0-) = 0$ 

Voltage across capacitor is voltage across  $R_2$ 

$$v_c(0-) = i_1(0-) \times 10 = 3.33 \times 10 = 33.33V$$

When switch is closed at  $t = 0.20 \Omega$  is short circuited. Inductor acts as current source with a value of 3.33 A and capacitor acts as voltage source with a value of 33.33 V which is as shown in Figure 25(b).

$$i_2(0+) = \frac{100 - 33.33}{10} = 6.667$$

Apply KVL for the inductor branch

$$100 = 10i_1 + L \frac{di_1}{dt}$$

At  $t = 0^+$ 

$$10i_{1}(0^{+}) + L\frac{di_{1}(0^{+})}{dt} = 100$$
  
$$1\frac{di_{1}(0^{+})}{dt} = 100 - 10 \times 3.33$$
  
$$\frac{di_{1}(0^{+})}{dt} = 66.7A/sec$$

Apply KVL for the capacitor branch.

$$100 = 10i_2 + \frac{1}{C} \int i_2 dt$$

At  $t = 0^+$ 

$$100 = 10i_2(0+) + \frac{1}{C}\int i_2(0+)dt$$

Differentiating we get

$$0 = 10 \frac{di_2(0+)}{dt} + \frac{1}{C}i_2(0+)$$
$$\frac{di_2(0+)}{dt} = -\frac{1}{10 \times C}i_2(0+)$$
$$= -\frac{1}{10 \times 1 \times 10^{-6}} \times 6.667$$
$$= -0.667 \times 10^6 \text{ A/sec}$$

2014-JULY) In the circuit shown in Figure 26 the switch S is changed from position a to b at t = 0, steady state condition having been reached before switching. Find the values of i,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ .



Figure 26: 2014-JULY

When the switch is at position a, and at  $t = 0^-$  the circuit is as shown in Figure ??. When the steady state is reached, capacitor is fully charged with a capacitor voltage  $v_c(0^-) = 40V = v_c(0^+)$  and current in the circuit  $i_L(0^-) = 0 = i_L(0^+)$ .



Figure 27: 2014-JULY

At  $t = 0^+$  the circuit is redrawn and is as shown in Figure 28 (a).



#### Figure 28: 2014-JULY

At  $t > 0^+$  the circuit is redrawn and is as shown in Figure ?? (b).

$$Ri + L\frac{di}{dt} + \frac{1}{C}\int idt = 0$$
 (22)

$$Ri(0^{+}) + L\frac{di}{dt}(0^{+}) + \frac{1}{C}\int i(0^{+})dt = 0$$
  
$$20 \times 0 + 1\frac{di}{dt}(0^{+}) + 20 = 0$$
  
$$\frac{di}{dt}(0^{+}) = -20A/sec$$

Differentiating equation 22

$$R\frac{di}{dt} + L\frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

Substituting initial conditions

$$R\frac{di}{dt}(0^{+}) + L\frac{d^{2}i}{dt^{2}}(0^{+}) + \frac{i(0^{+})}{C} = 0$$
  
$$20 \times (-20) + 1\frac{d^{2}i}{dt^{2}}(0^{+}) + \frac{0}{C} = 0$$
  
$$\frac{d^{2}i}{dt^{2}}(0^{+}) = 400A/sec^{2}$$

Q 2012-JULY-6b and 2013-DEC-6a) In the circuit shown in Figure 29 the switch K is changed from position 1 to 2 at t = 0, steady state condition having reached before switching. Find  $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$  at  $t = 0^+$ .

Solution:



Figure 29: 2013-JULY-6a-1

# Solution:

When switch is at position 1 and when steady state is reached inductor acts as short circuit which is as shown in Figure 30. At  $t = 0^-$ 



Figure 30: 2013-JULY-6a-1

Current cannot change instantaneously  $i(0^+) = i(0^-) = 2A$ , at  $t = 0^+$  the circuit is as shown in Figure 31

$$30i + L\frac{di}{dt} = 0$$
  

$$30i(0^{+}) + L\frac{di(0^{+})}{dt} = 0$$
  

$$\frac{di(0^{+})}{dt} = -30i(0^{+}) = -30 \times 2$$
  

$$= -60 \ A/sec$$

Differentiating

$$\frac{d^2 i(0+)}{dt^2} = -\frac{30 di(0^+)}{dt}$$
  
= -30 × (-60)  
= 1800 A/sec<sup>2</sup>



Figure 31: 2013-JULY-6a-1

Q 2013-DEC-6b) In the circuit shown in Figure 32 the switch K is opened at t = 0. Find v,  $\frac{dv}{dt}$ ,  $\frac{d^2v}{dt^2}$  at  $t = 0^+$ .



Figure 32: 2013-JULY-6a-1

#### Solution:

The switch is closed at  $t = 0^-$ . When switch is opened at t = 0 and which is as shown in Figure ??. At  $t = 0^-$ 

$$v(0^{-}) = 0 = v(0^{+})$$



 $\label{eq:Figure 33: 2013-JULY-6a-1}$  At  $t \geq 0^+$  the circuit is as shown if Figure 34



Figure 34: 2013-JULY-6a-1

$$\frac{V(t)}{R} + C\frac{dV(t)}{dt} = I$$

$$\frac{V(0^+)}{R} + C\frac{dV(0^+)}{dt} = 10$$

$$\frac{dV(0^+)}{dt} = \frac{10}{1 \times 10^{-6}}$$

$$= 10 \times 10^6 V/sec$$

Differentiating

$$\frac{1}{R}\frac{dV(t)}{dt} + C\frac{d^2V(t)}{dt^2} = 0$$

$$\frac{1}{R}\frac{dV(0^+)}{dt} + C\frac{d^2V(0^+)}{dt^2} = 0$$

$$\frac{d^2V(0^+)}{dt^2} = -\frac{1}{RC}\frac{dV(0^+)}{dt}$$

$$= -\frac{10 \times 10^6}{100 \times 1 \times 10^{-6}}$$

$$= -1 \times 10^{12} V/sec^2$$

Q 2013-JULY-6c ) In the circuit shown in Figure 35 the switch K is closed at t=0, all capacitor voltages and inductor currents are zero. Find  $v_1, v_2, v_3, \frac{dv_1}{dt}, \frac{dv_2}{dt}, \frac{dv_3}{dt}$  at  $t=0^+$ .



Figure 35: 2013-JULY-6c

Solution:



Figure 36: 2013-JULY-6c

When switch K is closed at t = 0 Capacitors  $C_1, C_2$  and  $C_3$  acts as a short circuit and inductors  $L_1$  and  $L_3$  acts as a open circuit.

KCL for node  $V_1$  and at  $t = 0^+$ 

$$\frac{V_1 - v(t)}{R_1} + C_1 \frac{dV_1}{dt} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1 - v(0^+)}{R_1} + C_1 \frac{dV_1(0^+)}{dt} + \frac{V_1(0^+) - V_2(0^+)}{R_2} = 0$$

$$\frac{0 - v(0^+)}{R_1} + C_1 \frac{dV_1(0^+)}{dt} + \frac{0 - 0}{R_2} = 0$$

$$\frac{dV_1(0^+)}{dt} = \frac{v(0^+)}{C_1R_1}$$

KCL for node  $V_2$  and at  $t = 0^+$ 

$$\frac{V_2 - V_1}{R_2} + C_2 \frac{dV_2}{dt} + \frac{1}{L_2} \int (V_2) dt = 0$$
  
$$0 + C_2 \frac{dV_2(0^+)}{dt} + L_2 \int (V_2(0^+)) dt = 0$$
  
$$\frac{dV_2(0^+)}{dt} = 0$$

KCL for node  $V_3$  and at  $t = 0^+$ 

$$\frac{1}{L_1} \int (V_3 - V_1) dt + C_3 \frac{dV_3}{dt} + = 0$$
  
$$\frac{1}{L_1} \int (V_3(0^+) - V_1(0^+)) dt + C_3 \frac{dV_3(0^+)}{dt} + = 0$$
  
$$\frac{dV_3(0^+)}{dt} = 0$$

Q 2011-DEC-6b) In the circuit shown in Figure 37 the switch K is closed at t = 0. Find i,  $\frac{di_1}{dt}$ ,  $\frac{d_1^2}{dt^2}$ ,  $\frac{di_2}{dt}$ ,  $\frac{d_2^2}{dt^2}$  at  $t = 0^+$ .



Figure 37: 2013-JULY-6a-1

Solution:

At  $t = 0^-$ 

$$v_c(0^-) = 0 = v(0^+)$$

$$i_1(0^-) = i_2(0^-) = i_2(0^+) = 0$$

The switch is closed at t = 0 and at  $t = 0^+$  the circuit is as shown in Figure 37.

$$i_1(0^+) = \frac{10}{10} = 1A \quad i_2(0^+) = 0A$$



Figure 38: 2013-JULY-6a-1



Figure 39: 2013-JULY-6a-1

Applying KVL for the loops

$$\frac{1}{C}\int i_1(t)dt + 10[i_1(t) - i_2(t)] = 10$$
 (23)

$$10[i_2(t) - i_1(t)] + 10i_2(t) + 1\frac{di_2}{dt} = 0$$
 (24)

At  $t = 0^+$  the equation 24 becomes

$$10[i_{2}(0^{+}) - i_{1}(0^{+})] + 10i_{2}(0^{+}) + 1\frac{di_{2}(0^{+})}{dt} = 0$$
  
$$10[0 - 1] + 10 \times 0 + 1\frac{di_{2}(0^{+})}{dt} = 0$$
  
$$\frac{di_{2}(0^{+})}{dt} = 10$$

Differentiating Equation 23

$$\frac{i_1}{C} + 10\left[\frac{di_1}{dt} - \frac{di_2}{dt}\right] = 0 \tag{25}$$

At  $t = 0^+$ 

$$\frac{i_1(0^+)}{C} + 10[\frac{di_2(0^+)}{dt} - \frac{di_2(0^+)}{dt}] = 0$$

$$\frac{i_1(0^+)}{C} + 10\left[\frac{di_1(0^+)}{dt} - \frac{di_2(0^+)}{dt}\right] = 0$$

$$\frac{1}{2 \times 10^{-6}} + 10\left[\frac{di_1(0^+)}{dt} - 10\right] = 0$$

$$10\frac{di_1(0^+)}{dt} = 100 - \frac{1}{2 \times 10^{-6}}$$

$$\frac{di_1(0^+)}{dt} = -49990 \ A/sec$$

Differentiating Equation 24

$$10\frac{di_2}{dt} - 10\frac{di_1}{dt} + 10\frac{di_2}{dt} + 1\frac{d^2i_2}{dt^2} = 0 \qquad (26)$$

At 
$$t = 0^+$$
  

$$\frac{d^2 i_2(0^+)}{dt^2} = -10 \times 10 + 10 \times (-49990) - 10 \times 10$$

$$\frac{d^2 i_2(0^+)}{dt^2} = -500100 \ A/sec^2$$

Differentiating Equation 25

$$\frac{1}{C}\frac{di_1}{dt} + 10\frac{d^2i_1}{dt^2} - 10\frac{d^2i_2}{dt^2} = 0$$
  
At  $t = 0^+$   
$$10\frac{d^2i_1(0^+)}{dt^2} = 10\frac{d^2i_2(0^+)}{dt^2} - \frac{1}{2\times 10^6}\frac{di_1(0^+)}{dt}$$
  
$$\frac{d^2i_1(0^+)}{dt^2} = -50010 - 0.5 \times 10^5(-49990)$$
  
$$\frac{d^2i_1(0^+)}{dt^2} = 2.499 \times 10^9 \ A/sec^2$$

Q 2020-JULY-6a, 2011-JULY-6c) Determine  $V, \frac{dV}{dt}, \frac{d^2V}{dt^2}$  at  $t = 0^+$  when the switch K is opened at t = 0 for the circuit shown in Figure 40.



Figure 40: 2011-JULY-6C1

# Solution:

At  $t = 0^-$  the switch is closed

$$i_L(0^-) = 0$$

= 10 A/s  $At = 0^+$  the switch is open which is as shown in Figure 41

At 
$$t \ge 0^+$$
 the s is as shown in Figure 42

Figure 42: 2011-JULY-6C1

$$\frac{V(t)}{R} + \frac{1}{L}\frac{1}{C}\int V(t)(t)dt = 2$$
 (27)

Differentiating Equation 27

$$\frac{1}{R}\frac{dV(t)}{dt} + \frac{1}{L}V(t) = 0$$

At  $t = 0^+$ 

$$\frac{1}{R}\frac{dV(0^+)}{dt} + \frac{1}{L}V(0^+) = 0$$

$$\frac{1}{R}\frac{dV(0^{+})}{dt} + \frac{1}{L}V(0^{+}) = 0$$
  
$$\frac{1}{200}\frac{dV(0^{+})}{dt} = -\frac{1}{L}V(0^{+}) = -400V$$
  
$$\frac{dV(0^{+})}{dt} = -\frac{1}{L}V(0^{+}) = -8 \times 10^{4}V/sec$$

Differentiating

$$\frac{1}{R}\frac{d^2v(t)}{dt^2} = \frac{1}{L}\frac{dV(t)}{dt}$$

At 
$$t = 0^+$$
  
$$\frac{1}{R} \frac{d^2 v(0^+)}{dt^2} = \frac{1}{L} \frac{dV(0^+)}{dt}$$

$$\frac{d^2v(0^+)}{dt^2} = 200 \times 8 \times 10^4 = 16 \times 10^4 V/sec^2$$

Q Prep-Q1 ) In Figure 47 the switch was closed Q Prep-Q1 ) In Figure 47 the switch was closed  $i_1(0^-), i_2(0^-), i_1(0^+)i_2(0^+).$ 



Figure 43: Prep-Q1

# Solution:

At  $t = 0^-$  the switch was closed and the modified circuit is as shown in Figure 44



Figure 44: Prep-Q1

The impedance of the circuit is

$$R_{eq} = 15 + \frac{15 \times 15}{15 + 15} k\Omega$$
  
= 15 + 7.5 = 22.5k\Omega

Total current supplied form the battery is

$$I = \frac{9}{R_{eq}} = \frac{9}{22.5k\Omega} \ 0.4mA$$

$$i_1(0^-) = 0.4mA \frac{15}{15+15} \ 0.2mA$$
  
 $i_2(0^-) = 0.4mA \frac{15}{15+15} \ 0.2mA$ 

At  $t = 0^+$  the switch is open

$$i_1(0^+) = 0.2mA$$
  
 $i_2(0^+) = -0.2mA$ 

for a long time before it is opened at t=0. Find for a long time before it is opened at t=0. Find  $i_1(0^-), i_2(0^-) i_1(0^+)i_2(0^+).$ 



Figure 45: Prep-Q1

Solution:

Q Prep-Q1 ) In Figure 47 the switch was closed for a long time before it is opened at t=0. Find  $i_1(0^-), i_2(0^-), i_1(0^+)i_2(0^+).$ 



Figure 46: Prep-Q1

Solution:

Q Prep-Q1 ) In Figure 47 the switch was closed for a long time before it is opened at t=0. Find  $i_1(0^-), i_2(0^-), i_1(0^+)i_2(0^+).$ 



Figure 47: Prep-Q1

Solution: