# 0.1 Millman's Theorem

#### Statement:

In a network if it contains a several voltage sources  $E_1$ ,  $E_2$ ,  $E_3$ ... with an internal impedances  $Z_1$ ,  $Z_2$ ,  $Z_3$ ..., which are connected in parallel may be replaced by a single voltage source E with internal impedance Z, where E and Z are

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$

and

$$Z = \frac{1}{Y} = \frac{1}{Y_1 + Y_2 + Y_3}$$

Consider a network containing source  $E_1, E_2, E_3...$  with an internal impedances  $Z_1, Z_2, Z_3...$ ,

٩

which are connected in parallel is as shown in Figure 1.

## Figure 1

Replace the each voltage source by current source with its internal resistance connected in parallel, which is as shown in Figure 2





All the current source are added to form a single current source I where I

 $I = I_1 + I_2 + I_3$ 

Replace the impedances by a single impedance Z where Z is

$$Y = \frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$



Figure 3

Next the current source by voltage source E where E is

$$E = IZ = \frac{I_1 + I_2 + I_3}{\frac{1}{Z}} = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

and

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$
$$Y = \frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

 $Y = Y_1 + Y_2 + Y_3$ 

2019-JULLY State and explain Millman's theorem. 2019-JAN For the circuit shown in Figure 4 find the current through  $(6 + j8)\Omega$ , impedance using Millman's theorem.





Solution:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{10} = 0.1$$
  

$$Y_2 = \frac{1}{Z_2} = \frac{1}{j10} = -j0.1$$
  

$$Y_3 = \frac{1}{Z_3} = \frac{1}{-j10} = j0.1$$

$$Y = Y_1 + Y_2 + Y_3 = 0.1 - j0.1 + j0.1$$
  
= 0.1  
$$Z = \frac{1}{Y} = \frac{1}{0.1} = 10\Omega$$

$$E_1Y_1 = 415 \times 0.1 = 41.5$$
  

$$E_2Y_2 = 415\angle 120 \times -j0.1 = 415\angle 120 \times 0.1\angle -90$$
  

$$= 41.5\angle 30 = 36 + j20.75$$
  

$$E_3Y_3 = 415\angle 240 \times j0.1 = 41.5\angle 330$$
  

$$= 36 - j20.75$$

$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{41.5 + 36 + j20.75 + 36 - j20.75}{0.1}$   
=  $\frac{113.5}{0.1}$   
= 1135

# $Y_1 = \frac{1}{-} = \frac{1}{-} = 0.5$

 $2\Omega$ 

20 V

Solution:

$$Y_{2} = \frac{1}{Z_{2}} = \frac{1}{4} = 0.25$$
$$Y_{3} = \frac{1}{Z_{3}} = \frac{1}{5} = 0.2$$

Figure 6

Figure 5 The current through  $(6 + j8)\Omega$ , impedance is

 $I = \frac{E}{Z + Z_L} = \frac{1135}{10 + 6 + j8}$  $= \frac{1135}{16 + j8} = \frac{1135}{17.88\angle 26.56}$ 

2018-JULY Using Millman's theorem find current

≹5Ω

±)50 V

 $\begin{cases} I_{L} \\ R_{L} = 9.4\Omega \end{cases}$ 

 $= 63.47 \angle -26.56$ 

through  $R_L$  for the circuit shown in Figure 6.

**ξ**4Ω

40 V

$$Y = Y_1 + Y_2 + Y_3 = 0.5 + 0.25 + 0.2$$
  
= 0.95  
$$Z = \frac{1}{Y} = \frac{1}{0.95} = 1.052\Omega$$

Y

$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{20 \times 0.5 + 40 \times 0.25 + 50 \times 0.2}{0.95}$   
=  $\frac{30}{0.95}$   
= 31.57

Millman's equivalent circuit is is as shown in Figure

Millman's equivalent circuit is is as shown in 7. Figure 5.



The current  $I_L$  through  $R_L$  is

$$I_L = \frac{31.57}{Z + Z_L} = \frac{31.57}{1.052 + 9.4}$$
  
= 3.02A

2017-JAN Apply Millman's theorem to find  $V_O$  and  $I_O$  for the circuit shown in Figure 8.



Figure 8

Solution:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{10} = 0.1$$
  

$$Y_2 = \frac{1}{Z_2} = \frac{1}{-j5} = j0.2$$
  

$$Y_3 = \frac{1}{Z_3} = \frac{1}{j5} = -j0.2$$

$$Y = Y_1 + Y_2 + Y_3 = 0.1 + j0.2 - j0.2$$
  
= 0.1  
$$Z = \frac{1}{Y} = \frac{1}{0.1} = 10\Omega$$
$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_2}$$

$$= \frac{100 \times 0.1 + j100 \times j0.2 + j100 \times -j0.2}{0.1}$$
$$= \frac{-30}{0.1}$$
$$= -300$$

Millman's equivalent circuit is is as shown in Figure 7.



Figure 9

The current  $I_L$  through  $R_L$  is

$$I_L = \frac{-300}{Z + Z_L} = \frac{-300}{10 + 2}$$
  
= 25A  
$$V_O = 25 \times 2 = 50V$$

2014-JULLY Using Millman's theorem find the current  $I_L$  through  $R_L$  for the network shown in Figure 10.



Figure 10

Solution:

$$\begin{array}{rcl} Y_1 & = & \frac{1}{Z_1} = \frac{1}{2} = 0.5 \\ Y_2 & = & \frac{1}{Z_2} = \frac{1}{3} = 0.33 \\ Y_3 & = & \frac{1}{Z_3} = \frac{1}{4} = 0.25 \end{array}$$

$$Y = Y_1 + Y_2 + Y_3 = 0.5 + 0.33 + 0.25$$
  
= 1.0833  
$$Z = \frac{1}{Y} = \frac{1}{1.0833} = 0.923\Omega$$

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{10 \times 0.5 + 20 \times 0.33 + 30 \times 0.25}{1.0833}$   
=  $\frac{19.16}{1.0833}$   
= 17.689

Millman's equivalent circuit is is as shown in Figure 11.



Figure 11 The current  $I_L$  through  $R_L$  is

$$I_L = \frac{E}{Z + Z_L} = \frac{17.689}{17.689 + 10}$$
  
= 1.6191A

2013-JAN Using Millman's theorem find the current  $I_L$  through  $R_L$  for the network shown in Figure 12.



Figure 12

$$Y_1 = \frac{1}{Z_1}$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{4} = 0.25$$
  

$$Y_2 = \frac{1}{Z_2} = \frac{1}{4} = 0.25$$
  

$$Y_3 = \frac{1}{Z_3} = \frac{1}{4} = 0.25$$

$$Y = Y_1 + Y_2 + Y_3 = 0.25 + 0.25 + 0.25$$
  
= 0.75  
$$Z = \frac{1}{Y} = \frac{1}{0.75} = 1.333\Omega$$
  
$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{-4 \times 0.25 - 2 \times 0.25 + 10 \times 0.25}{0.75}$   
=  $\frac{1}{0.75}$   
= 1.333

Millman's equivalent circuit is as shown in Figure 13.



Figure 13



$$I_L = \frac{E}{Z + Z_L} = \frac{1.333}{1.333 + 10}$$
  
= 0.1176A

Figure 14.





Solution:

$$Y_1 = \frac{1}{Z_1}$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{1} = 1$$
  

$$Y_2 = \frac{1}{Z_2} = \frac{1}{2} = 0.5$$
  

$$Y_3 = \frac{1}{Z_3} = \frac{1}{3} = 0.333$$

$$Y = Y_1 + Y_2 + Y_3 = 1 + 0.5 + 0.333$$
  
= 1.833

$$Z = \frac{1}{Y} = \frac{1}{1.833} = 0.5454\Omega$$

$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{1 \times 1 + 2 \times 0.5 + 3 \times 0.333}{0.333}$   
=  $\frac{1}{1.833}$   
=  $1.636V$ 

Millman's equivalent circuit is as shown in Figure 15.



Figure 15 The current  $I_L$  through  $R_L$  is

$$I_L = \frac{E}{Z + Z_L} = \frac{1.636}{0.5454 + 10}$$
  
= 0.1552A

2013-JULY Using Millman's theorem find the 2012-JULY Using Millman's theorem find the current  $I_L$  through  $R_L$  for the network shown in current  $I_L$  through  $R_L$  for the network shown in Figure 16.



Figure 16

Solution:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{2} = 0.5$$
  

$$Y_2 = \frac{1}{Z_2} = \frac{1}{4} = 0.25$$
  

$$Y_3 = \frac{1}{Z_3} = \frac{1}{5} = 0.2$$

$$Y = Y_1 + Y_2 + Y_3 = 0.5 + 0.25 + 0.2$$
  
= 0.95

$$Z = \frac{1}{Y} = \frac{1}{0.95} = 1.052\Omega$$

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{20 \times 0.5 + 40 \times 0.25 + 50 \times 0.2}{0.95}$   
=  $\frac{30}{0.95}$   
=  $31.57V$ 

Millman's equivalent circuit is is as shown in Figure 17.



Figure 17

The current  $I_L$  through  $R_L$  is

$$I_L = \frac{E}{Z + Z_L} = \frac{31.57}{1.052 + 9.4}$$
  
= 3.02A

2012-JAN Using Millman's theorem determine voltage  $V_S$  of the network shown in Figure 18 given that  $E_R = 230\angle 0 V$ ,  $E_Y = 230\angle -120 V E_B = 230\angle 120 V$ .



Figure 18

Solution:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{j20} = -j0.05$$
$$Y_2 = \frac{1}{Z_2} = \frac{1}{-j20} = j0.05$$
$$Y_3 = \frac{1}{Z_3} = \frac{1}{20} = 0.05$$

$$Y = Y_1 + Y_2 + Y_3 = -j0.05 + j0.05 + 0.05$$
  
= 0.05

$$Z = \frac{1}{Y} = \frac{1}{0.05} = 20\Omega$$

$$E_1 Y_1 = 230 \times -j0.05 = -j11.5$$

$$E_2 Y_2 = 230\angle -120 \times j0.05$$

$$E_2 Y_2 = 230\angle -120 \times 0.05\angle 90 = 11.5\angle -30$$

$$E_3 Y_3 = 230\angle 120 \times 0.05 = -j11.5$$

$$E_3 Y_3 = 230\angle 120 \times 0.05 = 11.5\angle 120$$

$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{-j11.5 + 11.5\angle - 30 + 11.5\angle 120}{0.05}$   
=  $\frac{-j11.5 + 9.95 - j5.75 - 5.75 + j9.95}{0.05}$   
=  $\frac{4.2 - j7.3}{0.05} = \frac{8.42\angle - 60}{0.05}$   
=  $168.4\angle - 60V$ 

Millman's equivalent circuit is is as shown in Figure 19.



## Figure 19

Using Millman's theorem determine current flowing through  $(4 + j3) \Omega$  of the network shown in Figure 20



Figure 20

#### Solution:

Replace the current source and parallel resistance by a voltage source

$$Z_1 = 10 + j10 = 14.14\angle 45^{\circ}\Omega$$

$$E_1 = 10\angle 30 \times 14.14\angle 45^\circ = 141.4\angle 75^\circ$$

Similarly

$$Z_3 = 3 - j14 = 5\angle -53.13^{\circ}\Omega$$
$$E_3 = 4\angle -30 \times 5\angle -53.13^{\circ} = 20\angle -83.13^{\circ}$$

The modified network as shown in Figure 21



$$\begin{array}{rcl} Y_1 &=& \displaystyle \frac{1}{Z_1} = \frac{1}{14.14\angle 45^\circ} = 0.0707\angle -45^\circ \\ Y_1 &=& 0.05 - j0.05 \\ Y_2 &=& \displaystyle \frac{1}{Z_2} = \frac{1}{5} = 0.2 \\ Y_3 &=& \displaystyle \frac{1}{Z_3} = \frac{1}{5\angle -53.13^\circ} = 0.2\angle 53.13^\circ \\ &=& 0.12 + j0.16 \end{array}$$

$$Y = Y_1 + Y_2 + Y_3 0.12 + j0.16$$
  
= 0.37 + j0.11  
= 0.386\arrow 16.56

$$Z = \frac{1}{Y} = \frac{1}{0.386 \angle 16.56} = 2.6 \angle -16.56\Omega$$

$$E_1Y_1 = 141.14\angle 75 \times 0.0707\angle -45^\circ =$$
  
= 9.978\angle 30 = 8.641 + j4.989  
$$E_2Y_2 = 5\angle 30 \times 0.2 = 1\angle 30 = 0.8666 + j0.5$$
  
$$E_3Y_3 = 20\angle -83.13 \times 0.2\angle 53.13$$
  
= 4\angle - 30 = 3.464 - j2

$$E = \frac{E_1Y_1 + E_2Y_2 + E_3Y_3}{Y_1 + Y_2 + Y_3}$$
  
=  $\frac{8.641 + j4.989 + 0.8666 + j0.5 + 3.464 - j2}{0.386\angle 16.56}$   
=  $\frac{12.971 + j3.489}{0.386\angle 16.56} = \frac{13.432\angle 15}{0.386\angle 16.56}$   
=  $168.4\angle - 60V$ 

Millman's equivalent circuit is is as shown in Figure 19.



Figure 22

# 0.2 Thevenin's and Norton's Theorems

# 0.2.1 Thevenin's Theorem

# Statement:

Any linear, bilateral network with two terminals can be replaced by a single voltage source  $E_{TH}$  in series with an impedance  $Z_{TH}$ , where the  $E_{TH}$  is an open circuit voltage at the terminals and an impedance  $Z_{TH}$  is the equivalent impedance as viewed from the terminals into the network.



Figure 23

# **Proof:**

Consider a network as shown in Figure 24. The current in the terminal AB is





$$\frac{V-10}{2} + \frac{V}{4} + \frac{V}{18} = 0$$

$$V[0.5+0.25+0.0556] = 5$$

$$V = \frac{5}{0.8056} = 6.026$$

$$I_L = \frac{6.026}{18} = 0.3448A$$

• Step 1: Determine the Open Circuit Voltage





 $6i_1 - 10 = 0$ 

• Step 2: Determine the Tehevenin's Impedance



Figure 26

$$Z_{TH} = 8 + \frac{2 \times 4}{2+4} = 9.333\Omega$$

• Step 3: Tehevenin's Equivalent Circuit





# • Step 4: Current through $I_L$ is

$$i_1 = 1.666A$$
  
 $E_{TH} = 1.666A \times 4 = 6.667V$ 
 $I_L = \frac{E_{TH}}{Z_{TH} + Z_L} = \frac{6.667V}{9.333 + 10} = 0.344 A$ 



Figure 28

# 0.2.2 Norton's Theorem

#### Statement:

Any linear, bilateral network with two terminals can be replaced by a single current source  $I_N$  in parallel with an impedance  $Z_N$ , where the  $I_N$  is an short circuit current through the terminals and an impedance  $Z_N$  is the equivalent impedance as viewed from the terminals into the network.



Figure 29

# 0.2.3 Maximum Power Transfer Theorem

## Statement:

In Any linear, bilateral network maximum power is delivered to the load  $R_L$  by the source when the load resistance  $R_L$  is equal to the Thevenin's resistance  $R_{TH}$ .



Figure 30

Q 1) Find the Thevenin and Norton equivalent for the circuit shown in Figure 31 with respect terminals A-B



Figure 31

# Solution:

Determine the Thevenin voltage  $V_{TH}$ . Apply KVL for the circuit shown in Figure 32.



Figure 32

$$18x - 12y = 96$$
$$-12x + 28y = 0$$

By Solving

$$x = 7.467A$$
  $y = 3.2A$ 

$$V_{OC} = 7.467 \times 12A = 38.4V$$

$$Z_{TH} = [(6||12) + 4]||12 + 4$$
  
= [4 + 4]||12 + 4  
= 8||12 + 4 = 4.8 + 4  
= 8.8\Omega









$$18x - 12y + 0z = 96$$
  
-12x + 28y - 12z = 0  
$$0x - 12y + 16z = 0$$

By Solving

$$x = 9.212A$$
  $y = 5.818A$   $z = 4.36A$   
 $I_{SC} = I_N = z = 4.36A$ 



Figure 35

Current through  $R_L$  is

$$I_L = \frac{V_{OC}}{R_L} = \frac{38.4}{20 + 8.8} = 1.33A$$

Power through is

$$P_L = I_L^2 R_L = (1.33)^2 \times 20 = 35.56W$$

Maximum power is  $R_L$  is

$$I_L = \frac{V_{OC}}{R_N + R_L} = \frac{38.4}{8.8 + 8.8} = 2.18A$$

$$P_L = I_L^2 R_L = (2.18)^2 \times 8.8 = 41.856W$$

Q 2) Find the Thevenin and Norton equivalent for the circuit shown in Figure 36 with respect terminals A-B  $\,$ 



Figure 36

## Solution:

Determine the Thevenin voltage  $V_{TH}$ . Apply KVL for the for the circuit shown in Figure 37.

$$y = -2A$$
  

$$16x - 12y = 32$$
  

$$16x - 24 = 32$$
  

$$x = \frac{32 - 24}{16} = 0.5A$$

$$V_{OC} = 12[0.5A - (-2)].5A \times 3 = 30V$$



Figure 37

$$Z_{TH} = (4||12) + 1$$
  
= 3 + 1 = 4Ω







# Figure 39

Q 3) Find the Thevenin and Norton equivalent for the circuit shown in Figure 40 with respect terminals A-B  $\,$ 



Figure 40

# Solution:

Determine the Thevenin voltage  $V_{TH}$ . Apply the KVL for the circuit shown in Figure 41.

$$\begin{array}{rcl} 15x - 5y + & = & 50 \\ -5x + 10y & = & 0 \end{array}$$

By Solving

$$x = 4A \quad y = 2A$$
$$V_{OC} = 2A \times 3 = 6V$$



Figure 41





Figure 42

Determine the short circuit current by Applying KVL for the circuit 43

$$15x - 5y = 50$$
$$-5x + 7y = 0$$

By Solving

$$x = 4.375A$$
  $y = 3.125A$ 







Figure 44

Current through  $R_L$  is

$$I_L = \frac{V_{OC}}{R_L} = \frac{6}{1.92 + 10} = 0.503A$$

Power through is

$$P_L = I_L^2 R_L = (0.503)^2 \times 10 = 2.53W$$

Maximum power is  $R_L$  is

$$I_L = \frac{V_{OC}}{R_N + R_L} = \frac{6}{1.92 + 1.92} = 1.5625A$$
$$P_L = I_L^2 R_L = (1.5625)^2 \times 1.92 = 4.68W$$

Q 4) Find the Thevenin and Norton equivalent for the circuit shown in Figure ?? with respect terminals a-b



Figure 45

# Solution:

Determine the Thevenin voltage  $V_{TH}$ . Apply KVL for the circuit shown in Figure 46. By KVL around the loop

$$6i - 2i + 6i - 20 = 0$$
  

$$10i = 20$$
  

$$i = 2A$$

Voltage across AB  $V_{OC} = V_{TH}$  is

$$V_{OC} = 6i = 6 \times 2 = 12V$$





When dependant voltage sources are present then Thevenin Resistance  $R_{TH}$  is calculated by determining the short circuit current at terminals AB:



Figure 47

$$x - y = i_1$$

KVL for loop **x** 

$$12x - 2i_1 - 6y - 20 = 0$$
  

$$12x - 2(x - y) - 6y = 20$$
  

$$10x - 4y = 20$$

KVL for loop y

$$\begin{array}{rcl} -6x + 16y &=& 0\\ 6x - 16y &=& 0 \end{array}$$

Solving the following simultaneous equations

$$10x - 4y = 20 
6x - 16y = 0 
x = 2.353 y = 0.882 
I_{SC} = y = 0.882A$$

Thevenin's resistance is

$$R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{12}{0.882} = 13.6\Omega$$

The venin and Norton equivalent circuits as shown in Figure 48



Figure 48

Q 5) Find the Thevenin and Norton equivalent for the circuit shown in Figure 49 with respect terminals a-b



Figure 49

Solution:

Determine the Thevenin voltage  $V_{TH}$ . Apply the KVL for the circuit shown in Figure 50. From the figure it is observed that

 $i_a = -x$ 

By KVL for the loop **x** 

$$6x + 2i_a - 12 = 0$$
  

$$6x - 2x = 12$$
  

$$x = \frac{12}{4} = 3A$$
  

$$i_a = -x = -3A$$

Open Circuit voltage  $V_{OC}$  is

$$V_{OC} = 2i_a = 2 \times (-3) = -6V$$





When dependant voltage sources are present then Thevenin Resistance  $R_{TH}$  is calculated by determining the short circuit current at

terminals **AB**. Apply KVL for loop x

$$6x + 2i_a - 12 = 0$$
  

$$6x - 2x = 12$$
  

$$x = \frac{12}{4} = 3A$$
  

$$i_a = -x = -3A$$

Apply KVL for loop y

$$3y - 2i_a = 0$$
  

$$3y - 2(-3) = 0$$
  

$$y = \frac{-6}{2} = -2A$$

Short circuit current  $I_{SC}$ 

$$I_{SC} = y = -2A$$

The venin resistance is  $R_{TH}$ 

$$R_{TH} = \frac{-6}{-2} = 3\Omega$$



Figure 51

The venin's and Norton's Circuits are as shown in Figure 52



Figure 52

Q 6) Find the Thevenin and Norton equivalent for the circuit shown in Figure 53 with respect terminals a-b



# Figure 53

#### Solution:

Determine the Thevenin voltage  $V_{TH}$  for circuit shown in Figure 50. It is observed that

$$V_2 = 24$$
$$i_a = \frac{V_1}{8}$$



Figure 54

Apply (KCL) node voltage for the circuit shown in Figure 54 for node 1

$$\frac{V_1 - V_2}{2} + 4 + \frac{V_1}{8} + 3i_a = 0$$
  
$$\frac{V_1 - 24}{2} + 4 + \frac{V_1}{8} + 3\frac{V_1}{8} = 0$$
  
$$\frac{V_1}{2} + \frac{V_1}{8} + 3\frac{V_1}{8} = 8$$
  
$$V_1 = 8$$

To find the short current  $I_{sc}$  short the output terminals a and b.



Figure 55

When it is short circuited the current  $I_a = 0$  then dependent source becomes zero. The modified circuit is as shown in Figure 56.

$$\frac{V_1 - 24}{2} + 4 + I_{SC} = 0$$
  
$$\frac{0 - 24}{2} + 4 + I_{SC} = 0$$
  
$$I_{SC} = -4 + 12 = 8A$$



Figure 57

Q 7) Find the Thevenin and Norton equivalent for the circuit shown in Figure 58 with respect terminals a-b



Figure 58

Solution: Determine the Thevenin voltage  $V_{TH}$  by apply node voltage method for the circuit shown in Figure 59

$$\frac{V_1}{2k\Omega} + \frac{V_2}{40k\Omega} - 3 \times 10^{-3} = 0$$
  
$$0.5 \times 10^{-3}V_1 + 0.025 \times 10^{-3}V_2 = 3 \times 10^{-3}$$
  
$$0.5V_1 + 0.025V_2 = 3$$

It is observed that

$$V_a = V_1$$

$$V_1 - V_2 = 5V_a$$
$$V_1 - V_2 - 5V_a = 0$$
$$V_1 - V_2 - 5V_1 = 0$$
$$4V_1 + V_2 = 0$$

Solving following equations

$$\begin{array}{rcl} 0.5V_1 + 0.025V_2 &=& 3\\ 4V_1 + V_2 &=& 0 \end{array}$$

$$V_1 = 7.5V, V_2 = -30V$$



Figure 59

Determine the short circuit current  $I_{SC}$  for the circuit shown in Figure 60. It is observed that 40 k $\Omega$  is also shorted hence entire current is flowing through shortened terminals AB.

$$\begin{array}{rcl} x & = & 3mA \\ y & = & -x = -3mA \end{array}$$

$$\begin{array}{rcl} V_{OC} &=& -30V\\ Z_{TH} &=& \frac{V_{OC}}{I_{SC}} = \frac{-30V}{-3mA} = 10k\Omega \end{array}$$



Figure 60

The venin and Norton circuits are as shown in Figure 61



Q 8) Find the Thevenin and Norton equivalent for the circuit shown in Figure refThevenindependent8-1 with respect terminals a-b



#### Figure 62

#### Solution:

Determine the Thevenin voltage  $V_{TH}$  by applying KVL for the circuit shown in Figure 63. It is observed that there is a current source between two loops, hence apply supermesh analysis.

$$y - x = 5i = 5x$$
  

$$6x - y = 0$$
  

$$20x + 10y = 20$$

Solving the above equations

$$x = 0.25A$$
  $y = 1.5A$ 

$$V_{OC} = V_{TH} = 1.5A \times 8\Omega = 6V$$



#### Figure 63

Determine the  $I_{SC}$  for the circuit shown in Figure 64.

$$y - x = 5i = 5x$$
  

$$6x - y = 0$$
  

$$20x + 2y = 20$$

Solving the above equations

$$x = 0.625A$$
  $y = 3.75A$ 





$$Z_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{6}{3.75} = 1.6\Omega$$



Figure 65

Q 9) Find the Thevenin and Norton equivalent for the circuit shown in Figure 66 with respect terminals a-b  $\,$ 





## Solution:

Determine the Thevenin voltage  $V_{TH}$  for circuit shown in Figure 67. It is observed that

$$v_1 = \frac{V_C}{5} \times 1 = 0.2V_C$$

Apply KCL

$$\frac{V_C}{5} - 2 - \frac{v_1}{2} = 0$$

$$\frac{V_C}{5} - 2 - 0.2 \times \frac{V_C}{2} = 0$$

$$0.2V_C - 0.1V_C = 2$$

$$V_C = \frac{2}{0.1} = 20$$

$$V_{OC} = V_{TH} = V_C + 1 \times \frac{v_1}{2}$$
  
= 20 + 1 ×  $\frac{0.2 \times 20}{2}$   
= 22



Figure 67

Applying KCL for the circuit shown in Figure 68.

 $V_A = 0V$ 

$$\frac{V_C}{5} - 2 + \frac{V_C - V_A}{1} = 0$$
  
$$0.2V_C + 1V_C = 2$$
  
$$V_C = \frac{2}{1.2} = 1.67V$$

$$\begin{array}{rcl} \frac{V_A - V_C}{1} - \frac{v_1}{2} + I_{SC} &=& 0\\ & \frac{-V_C}{1} - \frac{0.2V_C}{2} &=& -I_{SC}\\ & \frac{1.67}{1} + \frac{0.2 \times 1.67}{2} &=& I_{SC}\\ & I_{SC} = 1.67 + 0.167 &=& 1.837A \end{array}$$



Figure 68



## Figure 69

By Test voltage method. Apply a test voltage of 1 V at the output terminals AB and determine the applied source current. The modified circuit is as shown in Figure 70.



Figure 70 It is observed that

$$v_1 = -1x = -x$$
$$y - x = \frac{v_1}{2} = \frac{-x}{2}$$
$$0.5x - y = 0$$

By supermesh analysis method

$$6x + 1 = 0$$
  

$$x = -\frac{1}{6} = -0167A$$
  

$$y = 0.5x = 0.5 \times (-0167A) = -0.0833A$$

The circuit impedance is

$$Z_{TH} = \frac{1V}{0.0833A} = 12\Omega$$

Q 9-1) Find the Thevenin and Norton equivalent for the circuit shown in Figure 71 with respect terminals a-b





#### Solution:

Determine the Thevenin voltage  $V_{TH}$  for circuit shown in Figure 72. It is observed that

$$v_x = \frac{V_C}{6} \times 3 = 0.5 V_C$$

Apply KCL

$$\frac{V_C}{6} - 10 - \frac{V_x}{4} = 0$$
  
$$\frac{V_C}{6} - 10 - \frac{0.5V_C}{4} = 0$$
  
$$V_C(0.166 - 0.125) = 10$$
  
$$0.0416V_C = 10$$
  
$$V_C = 240.38$$

$$V_{OC} = V_{TH} = V_C + 5 \times \frac{V_x}{4}$$
  
= 240.38 + 5 ×  $\frac{0.5V_C}{4}$   
= 240.38 + 5 ×  $\frac{0.5 \times 240.38}{4}$   
= 240.38 + 150 = 390.38



Figure 72 Applying KCL for the circuit shown in Figure 73.

$$V_A = 0V$$

$$\frac{V_C}{6} - 10 + \frac{V_C - V_A}{5} = 0$$
  

$$0.166V_C + 0.2V_C = 10$$
  

$$0.366V_C = 10$$
  

$$V_C = \frac{10}{0.366} = 27.27V$$

$$\begin{array}{rcl} \frac{V_A-V_C}{5}-\frac{V_x}{4}+I_{SC}&=&0\\ &&\frac{-V_C}{5}-\frac{0.5V_C}{4}&=&-I_{SC}\\ \frac{27.27}{5}+\frac{0.5\times27.27}{4}&=&I_{SC}\\ I_{SC}=5.454+3.408&=&8.862A \end{array}$$





$$Z_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{390.38}{8.862A} = 44\Omega$$





Q 10) Find the Thevenin equivalent for the circuit shown in Figure 75 with respect terminals a-b



Figure 75

# Solution:

For this circuit it does not have any independent sources. Apply a test voltage of 1 V at the output terminals AB and determine the applied source current. The modified circuit is as shown in Figure 76.



Figure 76

It is observed that

$$\begin{array}{rcl} i_x & = & -\frac{V_1}{2} \\ & = & -0.5V_1 \end{array}$$

Apply KCL for the node  $V_1$ 

$$\begin{aligned} +\frac{V_1}{4} + \frac{V_1}{2} + 2i_x - i_o &= 0\\ V_1[0.25 + .5] + 2(-0.5V_1) - i_o &= 0\\ V_1[0.25 + .5 - 1] - i_o &= 0\\ -0.25V_1 - i_o &= 0\\ -i_o &= 0.25V_1 \end{aligned}$$

$$R_{TH} = \frac{V_1}{i_o} = \frac{V_1}{0.25V_1} = 4\Omega$$





Q 11) Find the Thevenin equivalent for the circuit shown in Figure 78 with respect terminals a-b



Figure 78

# Solution:

Determine the Thevenin voltage  $V_{TH}$  for circuit shown in Figure 79.



Figure 79

$$x = 5$$

It is observed that

$$v_x = 4(x-y)$$
$$v_x = 20 - 4y$$

KVL for the mesh **z** 

$$-2v_x + 2(z - y) = 0$$
  
$$-2y + 2z - 2(20 - 4y) = 6y + 2z = 40$$

KVL for the mesh **y** 

$$4(y-x) + 2(y-z) + 6y = 0$$
  

$$-4x + 12y - 2z = 0$$
  

$$-4 \times 5 + 12y - 2z = 0$$
  

$$-20 + 12y - 2z = 0$$
  

$$12y - 2z = 20$$

Solving the following linear equations

$$12y - 2z = 20$$
  
 $6y + 2z = 40$   
 $y = 3.33A \ x = 10A$   
 $V_{OC} = 6y = 6 \times 3.33A = 20V$ 

Short circuit the output terminals AB and determine the short circuit current  $I_{SC}$ 





x = 5

It is observed that

$$v_x = 4(x-y)$$
$$v_x = 20 - 4y$$

KVL for the mesh **y** 

$$4(y-x) + 2(y-z) + 6y - 6k = 0$$
  

$$-4x + 12y - 2z - 6k = 0$$
  

$$-4 \times 5 + 12y - 2z - 6k = 0$$
  

$$-20 + 12y - 2z - 6k = 0$$
  

$$12y - 2z - 6k = 20$$

KVL for the mesh **z** 

$$2z - 2y - 2v_x = 0$$
  

$$-2y + 2z - 2(20 - 4y) = 0$$
  

$$-2y + 2z - 40 + 8y = 0$$
  

$$-2y + 2z - 2(20 - 4y) = 0$$
  

$$6y + 2z + 0k = 40$$

KVL for the mesh **k** 

$$-6y + 0z + 8k = 0$$

Solving the following equations

$$12y - 2z - 6k = 20$$
  

$$6y + 2z + 0k = 40$$
  

$$-6y + 0z + 8k = 0$$
  

$$y = 4.44, z = 6.667, k = 3.333$$
  

$$I_{SC} = k = 3.333$$
  

$$Z_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{20}{3.333} = 6\Omega$$

Alternative Method: To determine the short circuit current  $I_{SC}$ , apply a test voltage of 1 V at the output terminals AB and determine the applied source current  $i_o$ . The modified circuit is as shown in Figure 81.





It is observed that

$$v_x = -4y$$

Apply KVL for the mesh **x** 

$$-2v_x + 2(x - y) = 0$$
$$v_x = x - y$$
$$-4y = x - y$$
$$x = -3y$$

Apply KVL for the mesh y

$$-2x + 12y - 6z = 0$$
  
$$-2(-3y) + 12y - 6z = 0$$
  
$$18y - 6z = 0$$

Apply KVL for the mesh **z** 

$$-6y + 8z = -1$$

Solving the following simultaneous equations

$$18y - 6z = 0$$
  
-6y + 8z = -1  
$$y = -0.055, \ z = -0.166$$
  
$$i_O = -z = 0.166A$$
  
$$R_{TH} = \frac{V_O}{i_O} = \frac{1V}{0.166A} = 6\Omega$$

The Thevenin and Norton circuits are as shown in Figure 82



Figure 82

Q 13) Find the Thevenin equivalent for the circuit shown in Figure 83 with respect terminals a-b





Solution:

$$10I_x - 6I_x + 20 = 0$$
  

$$4I_x = -20$$
  

$$I_x = \frac{-20}{4} = -5A$$
  

$$V_{0,0} = -5A \times 6 = -30V$$





 $I_x = 0$ 

$$4I_x + 20 = 0$$
  

$$I_x = \frac{20}{4} = 5A$$
  

$$I_{SC} = 5A$$



Figure 85





Figure 86

Q 14) Find the Thevenin equivalent for the circuit shown in Figure 83 with respect terminals a-b





Solution:

$$7x - 20 = 0$$
  

$$x = \frac{20}{7} = 2.857A$$
  

$$V_{OC} = x \times 2 - 12$$
  

$$= 2.857 \times 2 - 12$$
  

$$= 6.29V$$



Figure 88

$$Z_{TH} = 8 + \frac{2 \times 5}{2 \times 5} \\ = 8 + \frac{10}{7} = 2.857A \\ = 9.43\Omega$$





A

#### Figure 90

Q 15) For the circuit shown in Figure 91 Find the Thevenin and Norton equivalent circuit with respect terminals A-B Solution:









$$V_A = \frac{50\angle 0^{\circ}}{5+j2} \times j2$$
  
= 18.57∠68.2°

$$V_B = \frac{50 \angle 90^{\circ}}{2 - j2} \times -j2$$
$$= 35.35 \angle 45^{\circ}$$

$$V_{AB} = V_A - V_B = 18.57\angle 68.2^\circ - 35.35\angle 45^\circ$$
  
= 19.69\angle - 156^\circ

$$Z_{AB} = \frac{5 \times j2}{5 + j2} + \frac{2 \times -j2}{2 - j2}$$
  
= (0.689 + j1.724) + (1 - j1) = 1.689 + j0.724

$$I_{AB} = \frac{V_{AB}}{Z_{AB} + 4}$$
  
=  $\frac{16.69 \angle 0^{-156}}{1.689 + j0.724 + 4}$   
=  $2.91 \angle -163.25^{\circ}$ 

Q 16) Find the Thevenin and Norton equivalent circuit between terminals A-B for the circuit shown in Figure 93.





Solution:











$$Z_{AB} = \left[ \left[ \frac{5 \times j5}{5 + j5} \right] + (2 + j3) \right] ||6$$
  
=  $\left[ (2.5 + j2.5) + (2 + j3) \right] ||6$   
=  $\left[ (4.5 + j5.5) \right] ||6$   
=  $3.31 + j1.4 = 3.6 \angle 23^{\circ}$ 

$$I_N = \frac{V_A}{2+j3} = \frac{18\angle 50.6^\circ}{2+j3} = 14.99\angle -5.71^\circ$$

Q 17) Find the Thevenin and Norton equivalent circuit between terminals A-B for the circuit shown in Figure 96.







Figure 97

$$I = \frac{50\angle 0^{\circ} - 25\angle 90^{\circ}}{8+j1} = 6.933\angle - 33.7^{\circ}$$

$$V_{AB} = 50\angle 0^{\circ} - 6.933\angle - 33.7^{\circ} \times (5+j5)$$
  
= 9.79\angle - 78.65^\circ



Figure 98

$$Z_{AB} = \frac{(5+j5) \times (3-j4)}{8+j1} = 4.23 - j1.15 \ \Omega$$