0.1 Star Delta Transformation





$$R_x + R_y = \frac{R_{xy}(R_{yz} + R_{zx})}{R_{xy} + R_{yz} + R_{zx}}$$
(1)

$$R_y + R_z = \frac{R_{yz}(R_{zx} + R_{xy})}{R_{xy} + R_{yz} + R_{zx}}$$
(2)

$$R_z + R_x = \frac{R_{zx}(R_{xy} + R_{yz})}{R_{xy} + R_{yz} + R_{zx}}$$
(3)

Equation (1)-(2)

$$R_x - R_z = \frac{R_{xy}R_{zx} - R_{yz}R_{zx}}{R_{xy} + R_{yz} + R_{zx}}$$
(4)

Equation (3)+(4)

$$2R_x = \frac{2R_{xy}R_{zx}}{R_{xy} + R_{yz} + R_{zx}}$$
$$R_x = \frac{R_{xy}R_{xz}}{R_{xy} + R_{yz} + R_{zx}}$$

Similarly

$$R_y = \frac{R_{yz}R_{yx}}{R_{xy} + R_{yz} + R_{zx}} \tag{6}$$

$$R_z = \frac{R_{zy}R_{zx}}{R_{xy} + R_{yz} + R_{zx}} \tag{7}$$

Star to Delta Transformation

$$R_x R_y = \frac{R^2_{xy} R_{xz} R_{yz}}{(\sum R_{xy})^2}$$
$$R_y R_z = \frac{R^2_{yz} R_{yx} R_{zx}}{(\sum R_{xy})^2}$$
$$R_z R_x = \frac{R^2_{zx} R_{yx} R_{yz}}{(\sum R_{xy})^2}$$

$$R_{x}R_{y} + R_{y}R_{z} + R_{z}R_{x} = \frac{R_{xy}R_{yz}R_{zx}(R_{xy} + R_{yz} + R_{zx})}{(\sum R_{xy})^{2}}$$

$$R_{x}R_{y} + R_{y}R_{z} + R_{z}R_{x} = \frac{R_{xy}R_{yz}R_{zx}(R_{xy} + R_{yz} + R_{zx})}{(\sum R_{xy})^{2}}$$
$$R_{x}R_{y} + R_{y}R_{z} + R_{z}R_{x} = \frac{R_{xy}R_{yz}}{\sum R_{yz}}R_{zx} = R_{x}R_{yz}$$

$$R_{yz} = \frac{R_x R_y + R_y R_z + R_z R_x}{R_x}$$
$$R_{yz} = R_y + R_z + \frac{R_y R_z}{R_x}$$
(8)

$$R_{xy} = R_x + R_y + \frac{R_x R_y}{R_z} \tag{9}$$

$$R_{zx} = R_z + R_x + \frac{R_z R_x}{R_y} \tag{10}$$

Q 1) 2020-Aug (2018 scheme ECE) 2020-Aug (2018 scheme EE) 2017-June Determine the Input resistance between PQ using star-delta transformation



Figure 2

Solution:

(5)

In the given circuit 6
$$\Omega$$
, 6 Ω and 18 connected
between A,B and C are in delta connection, convert
this into star network. The details are as shown in
Figure 3

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

Figure 3

In the circuit 5 Ω and 3.6 Ω are in series, 6 Ω and 1.2 Ω are in series and 3.6 Ω 18 Ω and 6 Ω are in series.



Figure 4

7.2 Ω 27.6 Ω are in parallel, which is in series with 8.6 $\Omega.$ The net resistance is.

$$R_{PQ} = 8.6 + \frac{7.2 \times 27.6}{7.2 + 27.6}$$

= 8.6 + 5.71
= 14.31\Omega

Q 2) For the circuit shown in Figure shown in Figure 5 determine the equivalent resistance between any two terminals. Solution:



Figure 5

Solution:

In the given 4, 4, 4, and Ω are in star network, convert this star network to delta network

 $R_{xy} = R_x + R_y + \frac{R_x \times R_y}{R_z} = 8 + 4 = 12\Omega$ $R_{xy} = 4 + 4 + \frac{4 \times 4}{4} = 8 + 4 = 12\Omega$ $R_{yz} = 4 + 4 + \frac{4 \times 4}{4} = 8 + 4 = 12\Omega$ $R_{zx} = 4 + 4 + \frac{4 \times 4}{4} = 8 + 4 = 12\Omega$

As shown in the Figure 6, by looking by any two terminals 12 Ω is parallel with 4 Ω

 $=\frac{12\times4}{12+4}=3\Omega$



Figure 6

By looking from XZ terminal the 3 Ω resistance is in parallel with series connection of 3 Ω and 3 Ω resistance.

$$R_{XZ} = \frac{3 \times 6}{3+6} = 2\Omega$$

Q 3) For the circuit shown in Figure shown in Figure 7 determine the equivalent resistance between (1)A and B and (2) A and N.



Figure 7

Solution:

Convert the internal star network to delta

No.

 $\mathbf{2}$

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

network

$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{AB} = 2 + 30 + \frac{2 \times 30}{4} = 32 + 15 = 47\Omega$$

$$R_{BC} = 4 + 30 + \frac{4 \times 30}{2} = 34 + 60 = 94\Omega$$

$$R_{CA} = 4 + 2 + \frac{4 \times 2}{30} = 6 + 0.266 = 6.266\Omega$$





In the circuit 10 Ω is parallel with 47 Ω

$$=\frac{10\times47}{10+47}=8.245\Omega$$

Similarly 94 Ω is parallel with 15 Ω

$$=\frac{94\times 15}{94+15}=12.93\Omega$$

Similarly 6 Ω is parallel with 6.266 Ω

$$=\frac{6\times 6.266}{6+6.266}=3.06\Omega$$

The details are as shown in Figure ??



Figure 9

While looking from terminal AB the resistances 12.93 and Ω and 3.06 Ω are in series and this resistance is parallel with 8.245 Ω

$$= 12.93 + 3.06 = 16\Omega$$

$$R_{AB} = \frac{8.245 \times 16}{8.245 + 16} = 5.44\Omega$$
 (ii) The resistance between A and N is



Figure 10

From the Figure 10 by looking from the terminal resistance between A and N, there is a delta network between NCB which is replaced by star network.

$$R_x = \frac{R_{xy}R_{xz}}{R_{xy} + R_{yz} + R_{zx}}$$

$$R_B = \frac{30 \times 15}{30 + 15 + 4} = 9.18$$

$$R_C = \frac{4 \times 15}{30 + 15 + 4} = 1.225$$

$$R_N = \frac{30 \times 4}{30 + 15 + 4} = 2.5$$



Figure 11

In the network of 6 Ω and 1.225 Ω are in series, 10 Ω and 9.18 Ω are in series. The details are as shown in Figure 12





Figure 13 The resistances 7.225 Ω and 19.18 Ω are in

3

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

parallel

$$=\frac{7.225\times19.18}{7.225\times19.18}=5.25\Omega$$

The details are as shown in Figure 14



Figure 14

The resistances 2.5 Ω and 5.25 Ω are in series. The resistances 2 Ω 7.75 Ω are in in parallel and the net resistance between A and N is

$$=\frac{2\times7.75}{2+7.75}=1.59\Omega$$

Q 4) Determine the equivalent resistance between terminals A and B



Figure 15

Solution:

$$R_A = \frac{4 \times 6}{20} = 1.2\Omega$$
$$R_B = \frac{4 \times 10}{20} = 2\Omega$$
$$R_C = \frac{6 \times 10}{20} = 3\Omega$$





18.667 Ω



Figure 17

$$R_{AB} = 1.2 + \frac{12.44 \times 18.667}{12.44 + 18.667} + 3.3\Omega$$

= 1.2 + $\frac{232.217}{12.44 + 31.187} + 3.3\Omega$
= 1.2 + 7.446 + 3.3 = 11.94 Ω

Q 5) 2018-Dec (2010 scheme) Find the resistance of the circuit shown in Figure shown in Figure 5 between A and B



Figure 18

Solution:

In the given network 18 there is delta network between xyz and it is replaced by star network.

$$R_X = \frac{20 \times 5}{40} = 2.5\Omega$$

$$R_Y = \frac{20 \times 15}{40} = 7.5\Omega$$

$$R_Z = \frac{15 \times 5}{40} = 1.875\Omega$$



Figure 19

In the circuit 19, 10 Ω 2.5 Ω are in series, similarly 5 Ω 7.5 Ω are in series. The details are as shown in Figure 20





In the circuit 20 at NPB 37.5 Ω 3.875 Ω and 30 are in delta connection, convert into star network. The details are as shown in Figure 21



Figure 21

In the circuit 21, 12.5 Ω , 2.045 Ω are in series, similarly 1.635 Ω 15 Ω are in series. The details are as shown in Figure 22



Figure 22

In the circuit 22 14.54 Ω , 16.63 Ω are in parallel, which is in series with similarly 15.76 Ω . The net resistance between AB is.

$$R_{AB} = 15.76 + \frac{14.54 \times 16.63}{14.54 + 16.63}$$

= 15.76 + 7.76
= 23.52\Overline{A}

Q 6) For the circuit shown in Figure shown in Figure 5 determine the current i using star delta transformation.

Solution:



Figure 23

As shown in Figure 23 there is delta network between ABC, convert this to star network





Figure 24

The resistances 0.333 Ω and 2 Ω are in series and 0.333 Ω and 1 Ω are in series.

The resistances 2.333 Ω and 1.333 Ω are in parallel its equivalent resistance is



Figure 25

$$=\frac{2.333\times1.333}{2.333+1.333}=\frac{3.109}{3.666}=0.848\Omega$$

Total network resistance is $1+0.333+0.848=2.181\Omega$

$$I = \frac{1}{2.181} = 0.458A$$

Q 7) Calculate the current in the 40 Ω resistance of the circuit shown in Figure shown in Figure 5 using star delta transformation.



5

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

Figure 26

Solution:

As shown in Figure 23 there is delta network between ABC, convert this to star network

$$R_A = \frac{20 \times 5}{30} = 3.333\Omega$$
$$R_B = \frac{5 \times 5}{30} = 0.833\Omega$$
$$R_C = \frac{20 \times 5}{30} = 3.333\Omega$$



Figure 27



Figure 28

The total resistance of the network is

$$= 3.333 + \frac{40.833 \times 3.333}{40.833 + 3.333} = 3.333\Omega$$
$$= 3.333 + \frac{136}{44.163} = 3.333 + 3.08 + \Omega$$
$$= 6.41\Omega$$

The total current flowing in the network is

$$I_1 = \frac{4}{6.41} = 0.624A$$

Using branch current division method the current in 40 Ω is

$$I_3 = 0.624A \frac{3.333}{44.163} = 0.047A$$

Q 8) Determine the currents supplied by the each battery using star-delta transformation



Figure 29

Solution:

As shown in Figure 29 there is delta network between ABC, convert this to star network

$$R_A = \frac{4 \times 6}{15} = 1.6\Omega$$
$$R_B = \frac{4 \times 5}{15} = 1.3\Omega$$
$$R_C = \frac{6 \times 5}{15} = 2\Omega$$

15



Figure 30

In the circuit 30, 3 Ω and 1.6 Ω are in series and also 2 Ω and 1.3 Ω are in series. The details are as shown in Figure 31





$$I_3 = I_1 + I_2$$

KVL for loop 1

$$15 - 4.6I_1 - 2I_3 = 0$$

$$15 - 4.6I_1 - 2I_1 - 2I_2 = 0$$

$$15 - 6.6I_1 - 2I_2 = 0$$

$$6.6I_1 + 2I_2 = 15$$

KVL for loop 2

$$20 - 3.3I_2 - 2I_3 = 0$$

$$20 - 3.3I_2 - 2I_1 - 2I_2 = 0$$

$$20 - 5.3I_2 - 2I_1 = 0$$

$$2I_1 + 5.3I_2 = 20$$

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

Simultaneous equations are

$$6.6I_1 + 2I_2 = 15 \tag{11}$$

$$2I_1 + 5.3I_2 = 20 \tag{12}$$

$$\Delta = \begin{vmatrix} 6.6 & 2\\ 2 & 5.3 \end{vmatrix} = 6.6 \times 5.3 - (2 \times 2) = 34.98 - 4$$

= 30.98

$$i_{1} = \frac{\begin{vmatrix} 15 & 2\\ 20 & 5.3 \end{vmatrix}}{\Delta} = \frac{79.5 - 40}{32.96} = \frac{39.5}{30.98} = 1.275A$$
$$i_{2} = \frac{\begin{vmatrix} 6.6 & 15\\ 2 & 20 \end{vmatrix}}{\Delta} = \frac{132 - 30}{30.98} = \frac{102}{30.98} = 3.292A$$

The current supplied by each battery are 1.275A and 3.292A respectively

9). Find the equivalent resistance between A and B as shown in Figure 33











$$R_{AB} = 1.87 + \frac{6.94 \times 3.55}{6.94 \times 3.55}$$

= 38 + 24.3 + 80 = 142.3\Overline{1}

0.2 Question Papers

Question Papers

2019-Jan (2017 scheme ECE) Find the equivalent resistance between a and b as shown in Figure 36 using star delta transformation



Figure 36: JAN-2019-Question Paper

Solution:

As shown in Figure 36 there is delta network between $8\Omega 5\Omega$ and 4Ω , convert this to star network

$$R_A = \frac{8 \times 5}{8 + 4 + 5} = 2.35\Omega$$
$$R_B = \frac{5 \times 4}{17} = 1.17\Omega$$
$$R_C = \frac{8 \times 4}{17} = 1.88\Omega$$







Figure 38 As shown in Figure 38 there is delta network between 6Ω 5.17 Ω and 5.35 Ω , convert this to star

network

$$R_A = \frac{6 \times 5.17}{6 + 5.17 + 5.35} = 1.87\Omega$$

$$R_B = \frac{5.17 \times 5.35}{16.52} = 1.67\Omega$$

$$R_C = \frac{6 \times 5.35}{16.52} = 1.94\Omega$$







Figure 40

$$R_{AB} = 1.87 + \frac{6.94 \times 3.55}{6.94 \times 3.55}$$

= 1.87 + 2.34 = 4.21\Omega

2019-DEC Determine the resistance between A and B of the network shown in Figure 41.



Figure 41: 2019-DEC

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

Solution:



Figure 42

As shown in Figure 42 there is delta network between $2\Omega \ 3\Omega$ and $6 \ \Omega$, convert this to star network

$$R_A = \frac{10 \times 30}{10 + 10 + 30} = 6\Omega$$
$$R_B = \frac{10 \times 30}{50} = 6\Omega$$
$$R_C = \frac{10 \times 10}{50} = 2$$







Figure 44

As shown in Figure 44 there is delta network between 6Ω 12.5 Ω and 24.5 Ω , convert this to star network

$$R_A = \frac{6 \times 12.5}{6 + 12.5 + 24.5} = 1.74\Omega$$

$$R_B = \frac{6 \times 24.5}{43} = 3.41\Omega$$

$$R_C = \frac{12.5 \times 24.5}{43} = 7.12\Omega$$





Figure 46

$$R_{AB} = 1.74 + \frac{9.41 \times 19.62}{9.41 \times 19.62} = 1.74 + 6.36$$
$$= 8.1\Omega$$

Also by observation its a wheatstone bridge because the ratio is

$$\frac{12.5}{12.5} = \frac{6}{6} = 1$$

Hence no current flows between E D

$$R_{AB} = \frac{25 \times 12}{25 \times 12} = 8.1\Omega$$

2019-DEC Determine the resistance between A and B of the network shown in Figure 41.



Figure 47: 2019-June-(2015-scheme-ECE)1 Solution:

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com



Figure 48

As shown in Figure 48 there is star network between $2\Omega \ 3\Omega$ and $5 \ \Omega$, convert this to star network

 $\begin{aligned} R_{AB} &= 2 + 3 + \frac{2 \times 3}{5} = 5 + 1.2 = 6.2\Omega \\ R_{AE} &= 2 + 5 + \frac{2 \times 5}{3} = 7 + 3.3 = 10.3\Omega \\ R_{BE} &= 5 + 3 + \frac{5 \times 3}{2} = 8 + 7.5 = 15.5\Omega \end{aligned}$



Figure 49





Figure 50

As shown in Figure 50 there is a delta network between $6.2\Omega \ 10.33\Omega$ and $6.07 \ \Omega$, convert this to star network

$$R_A = \frac{6.2 \times 10.33}{6.2 + 10.33 + 6.07} = 2.83\Omega$$

$$R_B = \frac{6.2 \times 6.07}{22.6} = 1.67\Omega$$

$$R_E = \frac{6.07 \times 10.33}{22.6} = 2.77\Omega$$



Figure 52

As shown in Figure 52 there is a delta network between 2.83Ω 6Ω and 10.77Ω , convert this to star network

$$R_A = \frac{2.83 \times 6}{19.6} = 0.87\Omega$$

$$R_E = \frac{2.83 \times 10.77}{19.6} = 1.55$$

$$R_D = \frac{10.77 \times 6}{19.6} = 3.3$$







Figure 54

$$= 0.87 + \frac{3.22 \times 7.3}{3.22 + 7.3} = 0.87 + 2.23$$
$$= 3.1\Omega$$

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

2018-Dec,2014-Dec Using star/delta transformation network determine the resistance between M and N of the network shown in Figure 55.



Figure 55: 2018-DEC-(2015-scheme-ECE)1 Solution:



Figure 56

As shown in Figure 56 there is delta network between $2\Omega \ 3\Omega$ and $6 \ \Omega$, convert this to star network











Figure 60

$$R_B = \frac{1.195 \times 9.43}{1.195 + 9.43} = 1.06\Omega$$

$$R_{MN} = 1 + 1.06 + 0.468 = 2.528\Omega$$

2015-Dec Find the equivalent resistance between A and B of the network shown in Figure 61 using Star-Delta transformation.



Figure 61: 2015-DEC

Solution:







As shown in Figure 62 there is delta network

🕲 ₁₁

between $9\Omega \ 9\Omega$ and $9 \ \Omega$, convert this to star network

$$R_A = \frac{15 \times 8}{28} = 4.28\Omega$$

$$R_D = \frac{5 \times 8}{28} = 1.42\Omega$$

$$R_C = \frac{15 \times 5}{28} = 2.67\Omega$$

$$R_B = \frac{9 \times 9}{27} = 3\Omega$$

$$R_E = \frac{9 \times 9}{27} = 3\Omega$$

$$R_F = \frac{9 \times 9}{27} = 3\Omega$$







Figure 64 15.67 and 14.42 Ω are in parallel

$$= \frac{15.67 \times 14.42}{15.67 \times 14.42} = 7.51\Omega$$

$$R_{AB} = 4.28 + 7.51 + 3 = 14.79\Omega$$

2013-DEC1 Using star/delta transformation determine the resistance between M and N of the network shown in Figure 65.



30Ω 30Ω 30Ω 30Ω 30Ω. 300 Figure 66: 2013-DEC1 :10Ω 10Ω 10Ω 0Ω -60Ω Figure 67: 2013-DEC1 10Ω 20Ω 10Ω 20Ω 10Ω В Figure 68: 2013-DEC1 10Ω 10Ω ξ40Ω 20Ω 13.33



Figure 69: 2013-DEC1

2008-June Using star/delta transformation determine the resistance between M and N of the network shown in Figure 70.



Figure 70: 2008-June

Solution:

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

Solution:



Figure 71: 2008-June

As shown in Figure 71 there is delta network between A C D 5 Ω 5 Ω and 10 Ω , and there is delta network between B C E 5 Ω 5 Ω and 10 Ω , convert this to star network

$$R_A = \frac{5 \times 5}{20} = 1.25\Omega$$

$$R_C = \frac{5 \times 10}{20} = 2.5\Omega$$

$$R_D = \frac{5 \times 10}{20} = 2.5\Omega$$

$$R_B = \frac{5 \times 5}{20} = 1.25\Omega$$

$$R_E = \frac{5 \times 10}{20} = 2.5\Omega$$

$$R_F = \frac{5 \times 10}{20} = 2.5\Omega$$



Figure 72: 2008-June22



Figure 73: 2008-June23



Figure 74: 2008-June24

$$R_{AB} = 1.25 + 3.33 + 1.25 = 5.83\Omega$$

2007-July Using star/delta transformation determine the resistance between A and B of the network shown in Figure 75.



Figure 75: 2007-July

Solution:

As shown in Figure 75 there is star network between 6Ω 6Ω and 6 Ω , convert this to star to delta network

$$R_{AB} = 6 + 6 + \frac{6 \times 6}{6} = 12 + 6 = 18\Omega$$

$$R_{AC} = 6 + 6 + \frac{6 \times 6}{6} = 12 + 6 = 18\Omega$$

$$R_{BC} = 6 + 6 + \frac{6 \times 6}{6} = 12 + 6 = 18\Omega$$



Figure 76: 2007-July 18 Ω between AC and AB are in parallel





В

$$AB = 18 + \frac{9 \times 9}{18} = 18 + 4.5 = 22.5\Omega$$

Dr. Manjunatha P Prof., Dept of ECE, JNN College of Engg Shimoga manjup.jnnce@gmail.com

Using star/delta transformation determine the resistance between A and B of the network shown in Figure 78.





Solution:



Figure 79





$$R_{PQ} = 7 + 7.785 + 2 = 16.785k\Omega$$

